



Cairo University
Faculty of Engineering

Department of Electronics and
Communications Engineering
ELC 3060 – Spring 2023



IC Analog Design

Mini project 2

Name:	Sec:	ID
شهيره اسامة شفيق محمد	2	9202725
محمد مصطفى محمد عبد الرحمن	3	9203343

1. Hand Analysis:


As we know $f_o = \sqrt{f_1 * f_2} = \sqrt{10 * 20} = 10\sqrt{2}$ MHz,

and to achieve symmetry $\rightarrow f_1 * f_2 = f_3 * f_4$ and

$$f_1 * f_2 = 200 \text{ \& } f_3 * f_4 = 150$$

So, to achieve symmetry we will change either the value of f_3 or f_4 but we noticed that if we changed f_4 we will get an attenuation less than 20 dB then we will change f_3 .
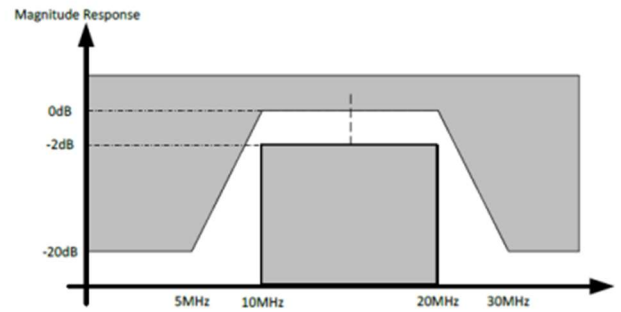
$$\text{So } f_3 = \frac{20}{3} \text{ MHz, and } \Omega_s = \frac{\omega_s}{\omega_p} = \frac{f_s}{f_p} = \frac{30 - \frac{20}{3}}{20 - 10} = \frac{7}{3}$$



The approximation that we used is **Chebyshev** as it's better in design than Butterworth

To get ϵ :

$$\rightarrow 10 \log_{10}(1 + \epsilon) = 2 \rightarrow \epsilon = 0.7647$$

To get order n :

$$\rightarrow 20 \log_{10}(\epsilon) + 20n \log_{10}(\Omega_s) + 6(n-1) = 20$$

$$n = \lceil 2.121 \rceil = 3 \rightarrow n = 3$$

To get transfer function :

$$\rightarrow \beta = \frac{1}{n} \sinh^{-1}\left(\frac{1}{\epsilon}\right) = 0.36105$$

$$\rightarrow S_k = \sinh(\beta) \sin\left(\frac{2k-1}{2n} \pi\right) + j \cosh(\beta) \cos\left(\frac{2k-1}{2n} \pi\right) \rightarrow k = 4, 5, 6$$

$$\rightarrow S_4 = -0.1845 + 0.923j$$

$$\rightarrow S_5 = -0.3689$$

$$\rightarrow S_6 = -0.1845 + 0.923j$$

$$\rightarrow \text{then } T(s) = \frac{1}{(s-S_4)(s-S_5)(s-S_6)} = \frac{0.3689*0.8859}{(s+0.3689)(s^2+0.369s+0.8859)} = \frac{0.3268}{s^3+0.7379s^2+1.022s+0.3268}$$

\rightarrow So, the transfer function of LPF is $\frac{0.3268}{s^3+0.7379s^2+1.022s+0.3268}$ and to transform it to BPF transfer function we used MATLAB for simplicity.

MATLAB code:

```
1 - w1=2*pi*10*10^6;
2 - w2=2*pi*20*10^6;
3 - w3=2*pi*(20/3)*10^6;
4 - W4=2*pi*30*10^6;
5 - W0=2*pi*14.14*10^6 ; %square root of W1*W2
6 - BW=w2-w1; %the bandwidth
7 - s=tf('s');
8 - H=(0.3268)/(s^3+0.7379*(s^2)+1.022*s+0.3268)
9 - A=0.3268;
10 - B=[1 0.7379 1.022 0.3268];
11 - [X,Y]=lp2bp(A,B,W0,BW);
12 - tf(X,Y)
13 - Poles=[1 4.636e07 2.771e16 8.13e23 2.188e32 2.889e39 4.918e47];
14 - roots(Poles) %to get the poles of BPF transfer function
```

BPF transfer function from MATLAB =

$$\frac{8.106 * 10^{22} s^3}{s^6 + 4.636 * 10^7 s^5 + 2.771 * 10^{16} s^4 + 8.13 * 10^{23} s^3 + 2.188 * 10^{32} s^2 + 2.889 * 10^{39} s + 4.918 * 10^{47}}$$

And the poles that we got from MATLAB are:

```
1.0e+08 *
-0.0757 + 1.2221i
-0.0757 - 1.2221i
-0.1160 + 0.8820i
-0.1160 - 0.8820i
-0.0400 + 0.6426i
-0.0400 - 0.6426i
```


- So, we will divide The BPF transfer function into second order transfer functions to be able to use Sallen Key filter for our design.
- Then the final transfer function will be as following:

$$TF = \frac{43278167.8 S}{s^2 + 0.1514 * 10^8 S + 1.5 * 10^{16}} * \frac{43278167.8 S}{s^2 + 0.232 * 10^8 S + 0.79183 * 10^{16}} * \frac{43278167.8 S}{s^2 + 0.08 * 10^8 S + 0.4145 * 10^{16}}$$

❖ We got the value of $43278167.8 S$ from $\sqrt[3]{8.106 * 10^{22} s^3}$

And the Sallen key BPF is as shown:

⇨ Sallen and Key Bandpass Filter

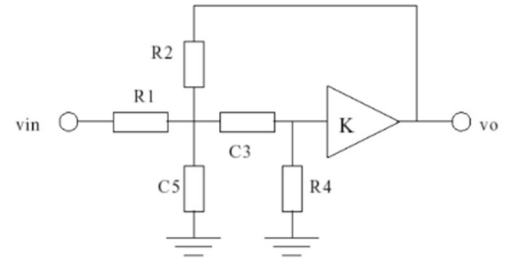

Design Equation:

$$\frac{\frac{K}{R1C5} S}{s^2 + \left(\frac{1}{R1C5} + \frac{1-K}{R2C5} + \frac{1}{R4C3} + \frac{1}{R4C5} \right) S + \frac{R1+R2}{R1 * R2 * R4 * C3 * C5}}$$

→ By solving the three transfer functions using the design equation, we got the values of R's and C's.

→ We assumed all the caps are equal to $\frac{100}{6}$ p F and k =3 then

$$R1 = \frac{3}{\frac{100}{6} * 10^{-12} * 43278167.8} = 4.15914 K\Omega \quad \frac{R1+R2}{R1 * R2 * R4 * C3 * C5} = 1.5 * 10^{16} \rightarrow (1)$$

$$\frac{1}{R1C5} + \frac{1-K}{R2C5} + \frac{1}{R4C3} + \frac{1}{R4C5} = 0.1514 * 10^8 \rightarrow (2) \quad \text{by solving (1) \& (2)}$$


We got $R2 = 520.4511 \Omega$ and $R4 = 518.84 \Omega$

Repeating same steps for stage 2 and 3 we got:


Stage 1	Stage 2	Stage 3
$R1 = 4.15914K\Omega$	$R1 = 4.15914K\Omega$	$R1 = 4.15914K\Omega$
$R2 = 520.4511\Omega$	$R2 = 752.6385\Omega$	$R2 = 1.01K\Omega$
$R4 = 518.84\Omega$	$R4 = 713.381\Omega$	$R4 = 1.068K\Omega$
$K = 3$	$K = 3$	$K = 3$
$C3 = C5 = \frac{100}{6} \text{ p F}$	$C3 = C5 = \frac{100}{6} \text{ p F}$	$C3 = C5 = \frac{100}{6} \text{ p F}$

2. Simulation:

I. Schematic:

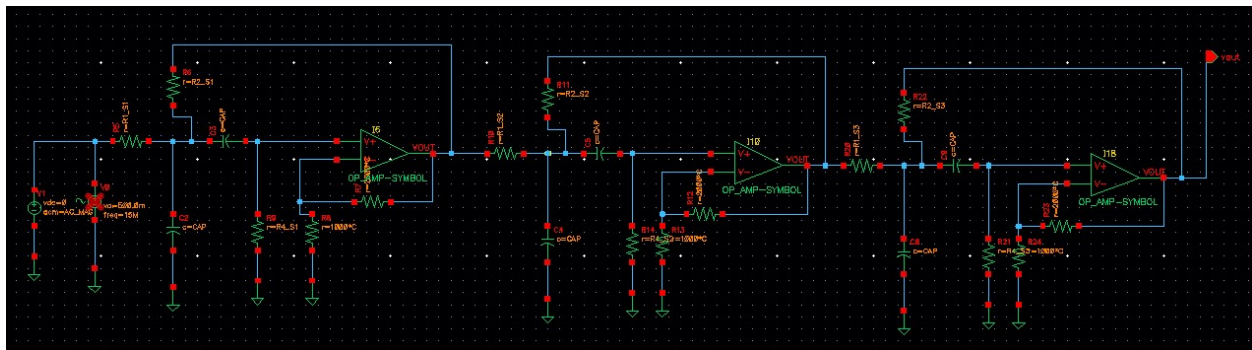

II. Ideal Op-Amp schematic:

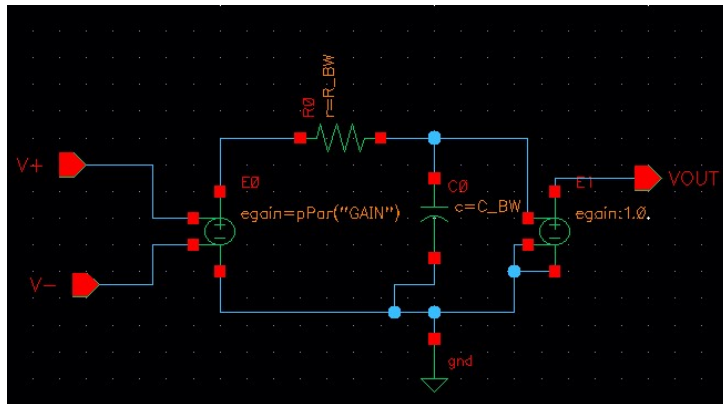


Data View	
<input checked="" type="checkbox"/> AC_MAG	1
<input checked="" type="checkbox"/> C_BW	0
<input checked="" type="checkbox"/> R_BW	0
<input checked="" type="checkbox"/> CAP	16.667p
<input checked="" type="checkbox"/> R1_S1	4.15914K
<input checked="" type="checkbox"/> R1_S2	4.15914K
<input checked="" type="checkbox"/> R1_S3	4.15914K
<input checked="" type="checkbox"/> R2_S1	520.4511
<input checked="" type="checkbox"/> R2_S2	752.6385
<input checked="" type="checkbox"/> R2_S3	1.01K
<input checked="" type="checkbox"/> R4_S1	518.84
<input checked="" type="checkbox"/> R4_S2	713.381
<input checked="" type="checkbox"/> R4_S3	1.068K
<input checked="" type="checkbox"/> C	1
<input checked="" type="checkbox"/> GAIN	10000
Click to add variable	

III. Ac Analysis:

Mag:


AC Analysis 'ac': freq = (1 Hz -> 10 GHz)

■ /vout ■ -30.512V 1.6667e+11

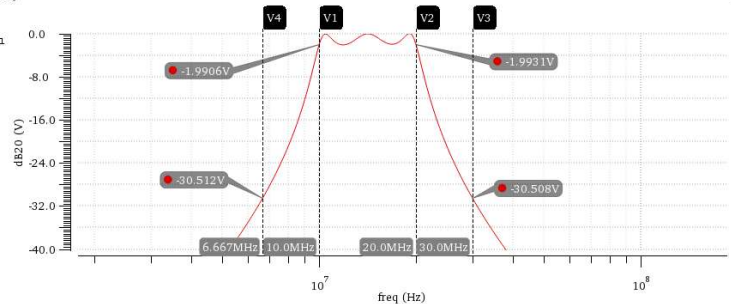

Phase:

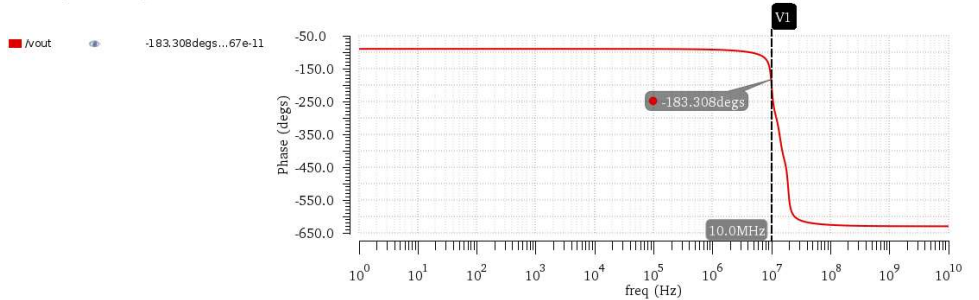AC Analysis 'ac': freq = (1 Hz -> 10 GHz)



IV. PZ Analysis:

Checking on Quality factor:

→ The first Stage:

$$S^2 + 0.1514 * 10^8 S + 1.5 * 10^{16}$$

$$\frac{\omega_o}{Q} = 0.1514 * 10^8 \text{ \&}$$

$$\omega_o = \sqrt{1.5 * 10^{16}} \rightarrow Q = 8.089$$

→ The second Stage:

$$S^2 + 0.232 * 10^8 S + 0.79183 * 10^{16}$$

$$\frac{\omega_o}{Q} = 0.232 * 10^8 \text{ \&}$$

$$\omega_o = \sqrt{0.79183 * 10^{16}} \rightarrow Q = 3.8355$$

→ The third Stage:

$$S^2 + 0.08 * 10^8 S + 0.4145 * 10^{16}$$

$$\frac{\omega_o}{Q} = 0.08 * 10^8 \text{ \&}$$

$$\omega_o = \sqrt{0.4145 * 10^{16}} \rightarrow Q = 8.0477$$

CAP_2=1.6667e-11

Poles (Hz)


	Real	Imaginary	Qfactor
Pole_1	-6.34056e+05	1.02304e+07	8.08288e+00
Pole_2	-6.34056e+05	-1.02304e+07	8.08288e+00
Pole_3	-1.84554e+06	1.40413e+07	3.83683e+00
Pole_4	-1.84554e+06	-1.40413e+07	3.83683e+00
Pole_5	-1.20404e+06	1.94549e+07	8.09448e+00
Pole_6	-1.20404e+06	-1.94549e+07	8.09448e+00

Zeros (Hz)

	Real	Imaginary	Qfactor
Zero_1	1.58439e-05	0.00000e+00	-5.00000e-01
Zero_2	-8.50123e+00	0.00000e+00	5.00000e-01
Zero_3	8.50127e+00	0.00000e+00	-5.00000e-01


Network function gain(magnitude)= 8.10656e+22

Poles and zeros locations:

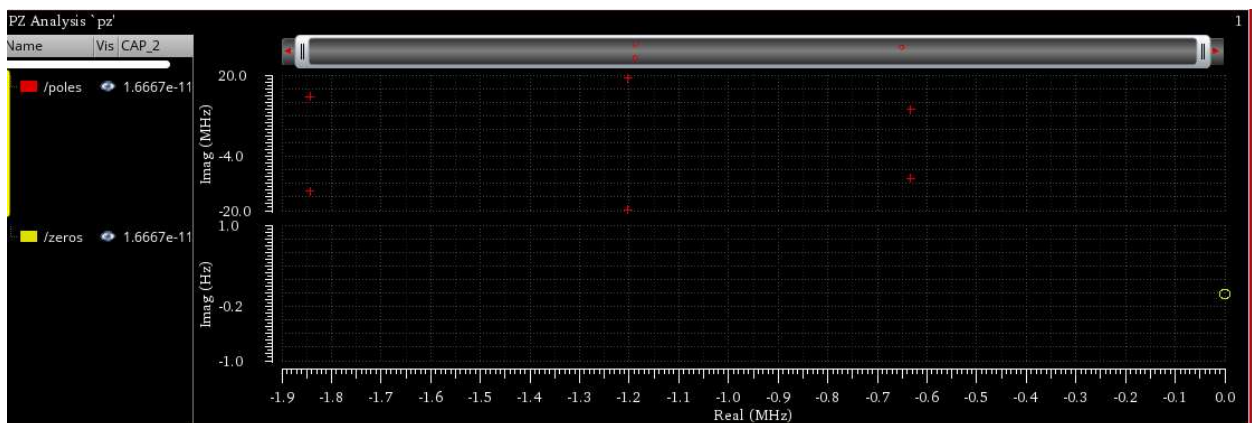


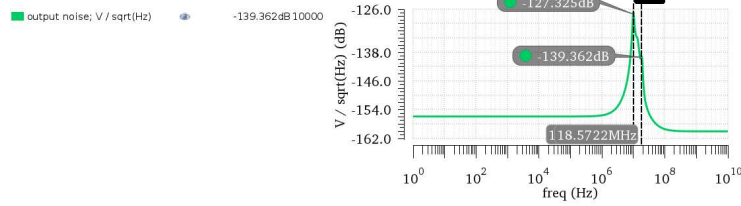V. Noise Analysis:

Noise Response 1 Noise Analysis 'noise': freq = (1 Hz -> 10 GHz)



In (dB)

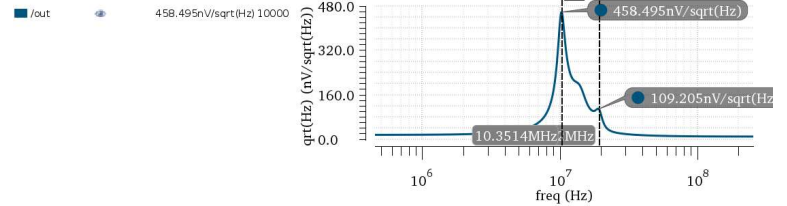

in (nV/sqrt(Hz))


VI. Noise Analysis (Reducing R's by factor 2):

To keep the transfer function unchanged by reducing Rs by factor 2 we will reduce the values of C's by 2 too.

Noise Analysis 'noise': freq = (1 Hz -> 10 GHz)

(nV/sqrt (Hz))

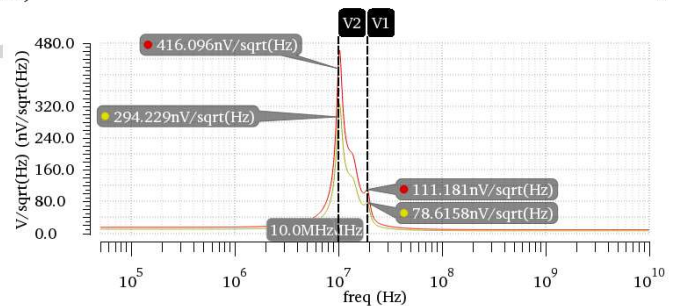
/out 111.181nV/sqrt(Hz) nom
/out 78.6158nV/sqrt(Hz) R/2



Noise Response

(dB)

output noise: V / sqrt(Hz)

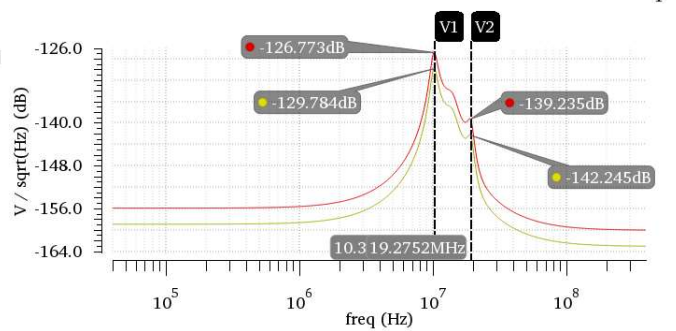

Comments:


- ➔ As shown in the figures when all resistors reduced by factor 2, the output referred noise also will be reduced by factor 2 because the thermal noise = $4KTR$.
- ➔ As R reduced by factor 2 the power consumption will be doubled (as the current increased) and the area will decrease to half.

VII. Transient Response:

Transient Analysis `tran`: time = (0 s -> 1 us)

1


Name	...	GAIN
/stage_1		10000
/stage_2		10000
/vin		10000
/vout		10000

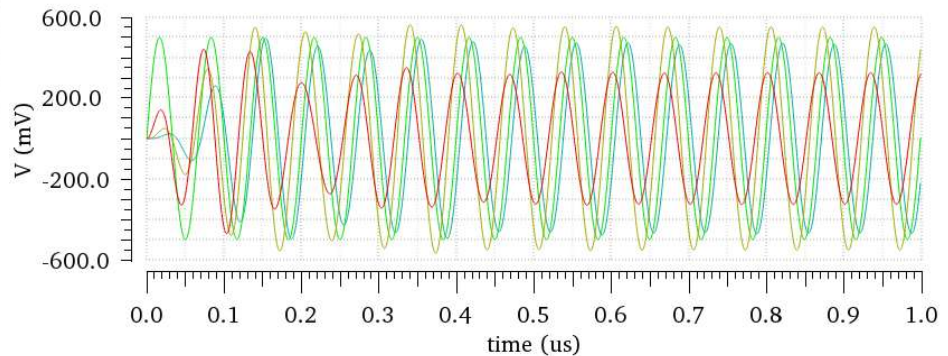

VIII. Discrete Fourier Transform:

db20(dft(value(v("/vout" ?result "tran") "GAIN" 10000) 100n 600n 1024 "Rectangular" 0 0 1))


2

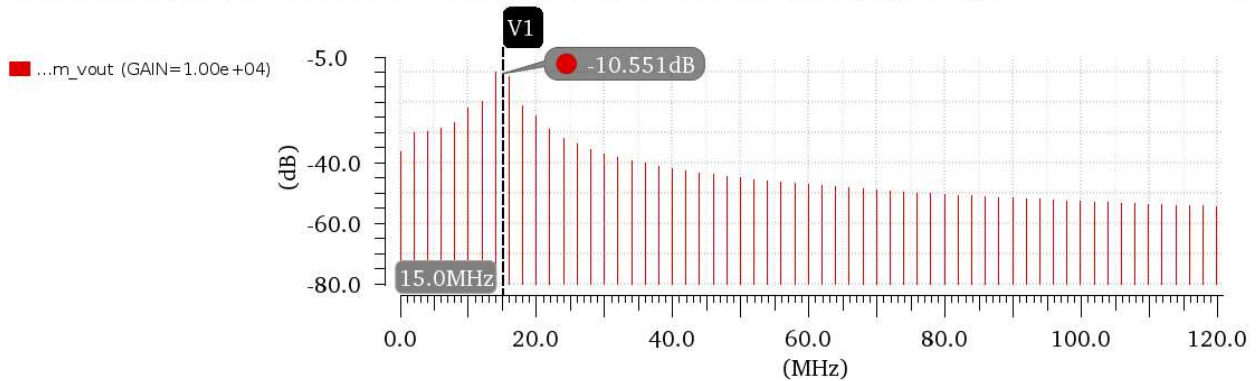

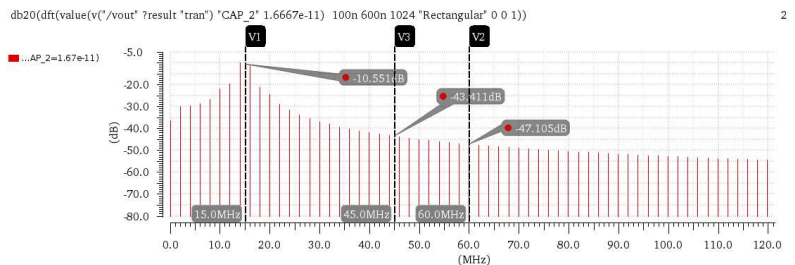IX. Third Harmonic distortion:

Comments:

- ➔ The fundamental harmonic is at 15 MHz is equal to -10.551 dB
- ➔ The third harmonic concluding the fundamental is at 45 MHz is equal to -43.411 dB
- ➔ Then the Third harmonic distortion in that case = $-43.411 - (-10.551) = -32.86$ dB
- ➔ The third harmonic after the fundamental is at 60 MHz is equal to -47.105 dB
- ➔ Then the Third harmonic distortion in that case = $-47.105 - (-10.551) = -36.554$ dB.




X. Varying all capacitors by $\pm 15\%$:



Comments:

- when all the caps are varying by +15% the bandwidth still the same but the maximum passband ripples started at frequency less than 10MHz. (As the caps increased)
- when all the caps are varying by -15% the bandwidth still the same but the maximum passband ripples started at frequency more than 10MHz. (As the caps decreased)

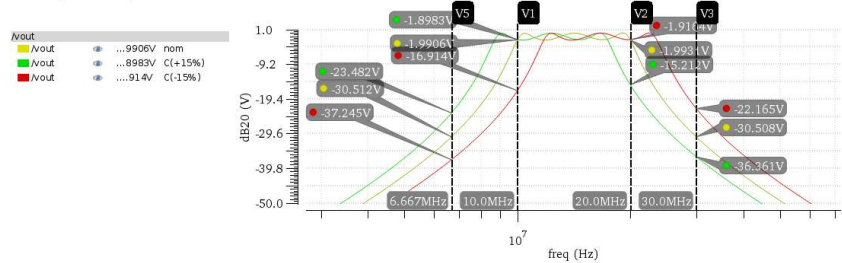AC Analysis 'ac': freq = (1 Hz -> 10 GHz)



The effect on Poles and zeros:

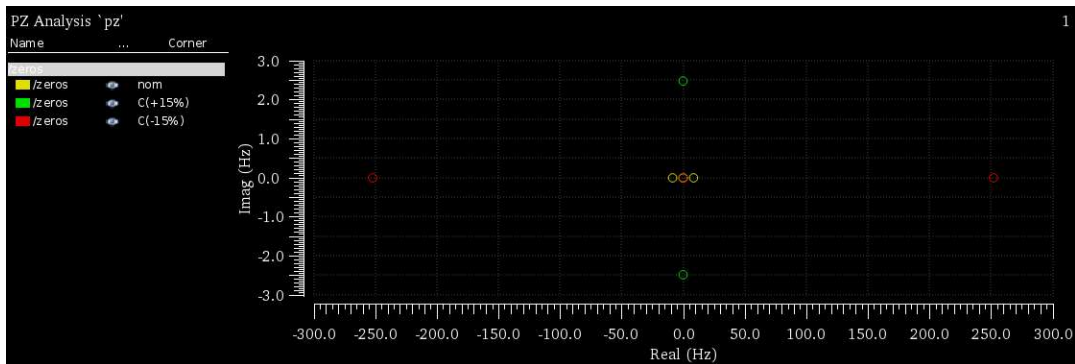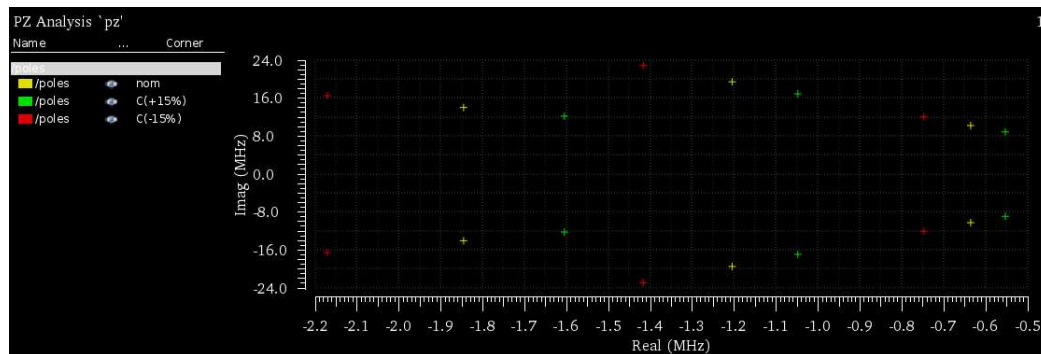

qfactor	/poles ...1 (Hz)	qfactor	/poles ...1 (Hz)	qfactor	/poles ...1 (Hz)	qfactor	/zeros ...1 (Hz)	qfactor	/zeros ...1 (Hz)	qfactor	/zeros ...1 (Hz)
1 8.083	12.06E6	8.083	10.25E6	8.083	8.913E6	500.0E-3	18.98E-6	-500.0E-3	15.84E-6	500.0E-3	15.24E-6
2 8.083	12.06E6	8.083	10.25E6	8.083	8.913E6	500.0E-3	252.4	500.0E-3	8.501	174.6E3	2.482
3 3.837	16.66E6	3.837	14.16E6	3.837	12.31E6	-500.0E-3	252.4	-500.0E-3	8.501	174.6E3	2.482
4 3.837	16.66E6	3.837	14.16E6	3.837	12.31E6						
5 8.095	22.93E6	8.094	19.49E6	8.095	16.95E6						
6 8.095	22.93E6	8.094	19.49E6	8.095	16.95E6						

	Varying c by +15	Varying c by -15
<u>Ap</u>	<u>-1.8983</u>	<u>-16.914 (bad)</u>
<u>As</u>	<u>-36.361</u>	<u>-22.165 (bad)</u>


XI. Varying capacitors of 1st stage by $\pm 2\%$:

Comments:

As shown in the figure the maximum passband ripples, and the minimum stopband attenuation are almost the same and the variation in the frequency is very small so the bandwidth still the same too.

AC Analysis 'ac': freq = (1 Hz -> 10 GHz)

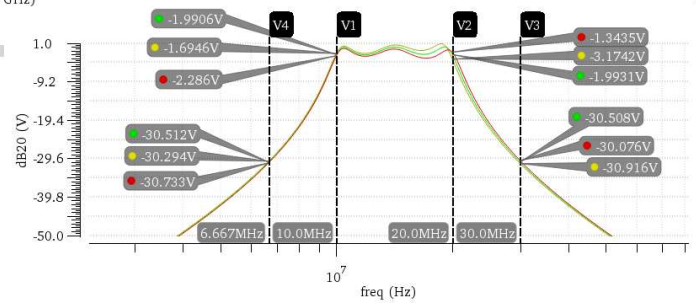
/vout
 /vout
 /vout
512V nom
294V C(+2%)
733V C(-2%)



The effect on Poles and zeros:


PZ Analysis 'pz'

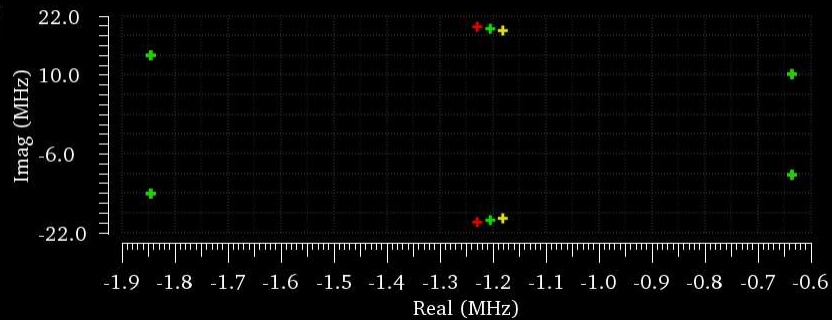Name Vis Corner
 /poles
 /poles nom
 /poles C(+2%)
 /poles C(-2%)



PZ Analysis 'pz'

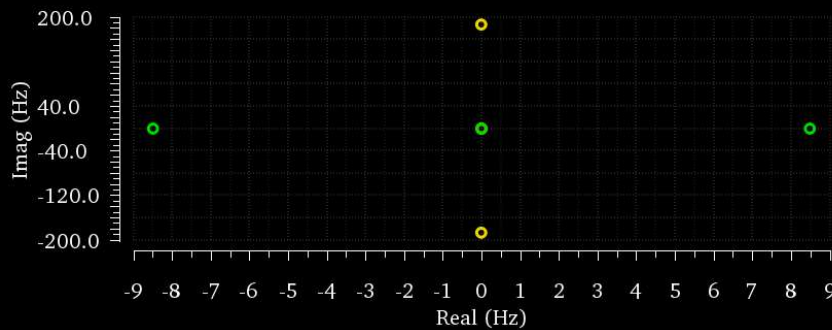Name Vis Corner
 /zeros
 /zeros nom
 /zeros C(+2%)
 /zeros C(-2%)



qfactor	/poles ...1 (Hz)	qfactor	/poles ...1 (Hz)	qfactor	/poles ...1 (Hz)	qfactor	/zeros ...1 (Hz)	/zeros ...1 (Hz)	qfactor	/zeros ...1 (Hz)
1 8.083	10.25E6	8.083	10.25E6	8.083	10.25E6	-500.0E-3	9.526E-6	3.528E-6	-500.0E-3	15.84E-6
2 8.083	10.25E6	8.083	10.25E6	8.083	10.25E6	19.13E3	186.7	186.7	500.0E-3	8.501
3 3.837	14.16E6	3.837	14.16E6	3.837	14.16E6	19.13E3	186.7	186.7	-500.0E-3	8.501
4 3.837	14.16E6	3.837	14.16E6	3.837	14.16E6					
5 8.095	19.89E6	8.095	19.11E6	8.094	19.49E6					
6 8.095	19.89E6	8.095	19.11E6	8.094	19.49E6					


	Varying c by +2	Varying c by -2
<u>Ap</u>	-1.6946	-2.286 (Bad)
<u>As</u>	-30.916	-30.076

XII. Varying the gain of the Op-amps to 1000 and 100:

Comments:

As shown in the figure when the gain of op-amp is decreased to 1000 the maximum passband ripples, and the minimum stopband attenuation is the same (that's because the gain is high and the op-amp acts as ideal Op-Amp but when the gain of op-amp is decreased to 100 the maximum passband ripples increased to 7.0782 dB, and the minimum stopband attenuation became 31.502dB and the transfer function will change too as the op-amp is no longer ideal.

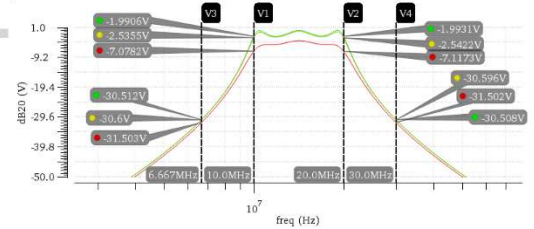AC Analysis 'ac': freq = (1 Hz -> 10 GHz)



XIII. Varying BW to 10MHz & 1MHz:

Comments:




As shown in the figure, at BW=10MHz specifications of the filter still the same for maximum passband and minimum stopband attenuation.

but for BW=1MHz (as we know the speed of op-amp depend on BW and since BW decreases to 1M then the speed decreases too)

The effect on Poles and zeros:

AC Analysis 'ac': freq = (1 Hz -> 10 GHz)

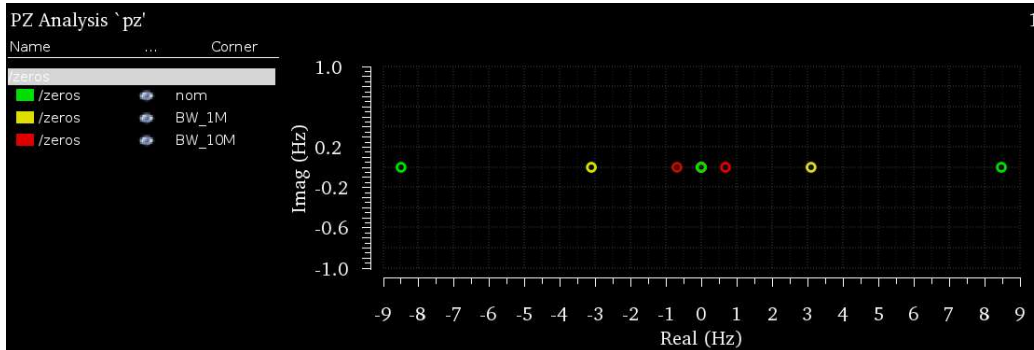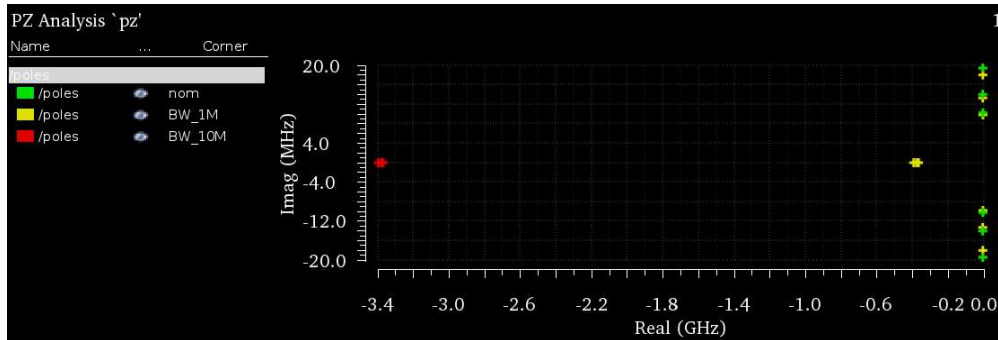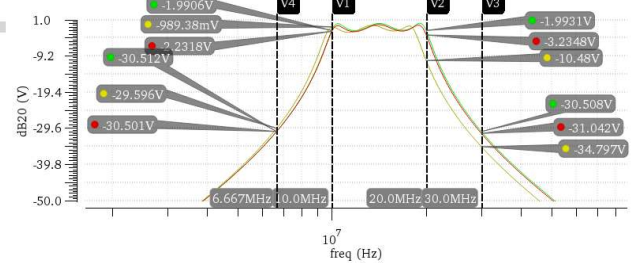Legend:
 /vout: -30.512V nom
 /vout: -29.596V BW_1M
 /vout: -30.501V BW_10M



qfactor	/poles ...0 (Hz)	qfactor	/poles ...0 (Hz)	qfactor	/poles ...0 (Hz)	qfactor	/zeros ...0 (Hz)	/zeros ...0 (Hz)	/zeros ...0 (Hz)
1 7.655	10.21E6	7.798	9.841E6	8.083	10.25E6	-500.0E-3	498.8E-6	621.3E-6	15.84E-6
2 7.655	10.21E6	7.798	9.841E6	8.083	10.25E6	500.0E-3	686.2E-3	3.111	8.501
3 3.754	14.08E6	3.878	13.41E6	3.837	14.16E6	-500.0E-3	686.2E-3	3.111	8.501
4 3.754	14.08E6	3.878	13.41E6	3.837	14.16E6				
5 7.682	19.33E6	7.743	18.06E6	8.094	19.49E6				
6 7.682	19.33E6	7.743	18.06E6	8.094	19.49E6				
7 500.0E-3	3.371E9	500.0E-3	362.6E6						
8 500.0E-3	3.380E9	500.0E-3	372.5E6						
9 500.0E-3	3.397E9	500.0E-3	389.3E6						

	Varying BW by 10M	Varying BW by 1M
Ap	-2.2318 (bad)	-98938
As	-31.042	-34.797